

[illegible]

VERILOG CODE

```


module encoder(a,y);
input [7:0]a;
output[2:0]y;

or(y[2],a[6],a[5],a[4],a[3]);
or(y[1],a[6],a[5],a[2],a[1]);
or(y[0],a[6],a[4],a[2],a[0]);

endmodule


```

OUTPUT WAVEFORM

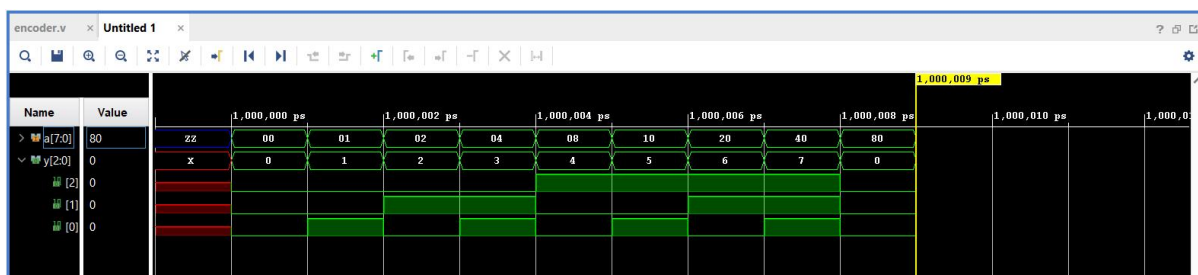

DECODER

LOGIC DIAGRAM

 

A2	A1	A0	D7	D6	D5	D4	D3	D2	D1	D0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

VERILOG CODE

```

module decoder1(a,y);
input [2:0]a;
output[7:0]y;

and(y[0],~a[2],~a[1],~a[0]);
and(y[1],~a[2],~a[1],a[0]);


```

```

and(y[2],~a[2],a[1],~a[0]);
and(y[3],~a[2],a[1],a[0]);
and(y[4],a[2],~a[1],~a[0]);
and(y[5],a[2],~a[1],a[0]);
and(y[6],a[2],a[1],~a[0]);
and(y[7],a[2],a[1],a[0]);
endmodule


```

OUTPUT WAVEFORM

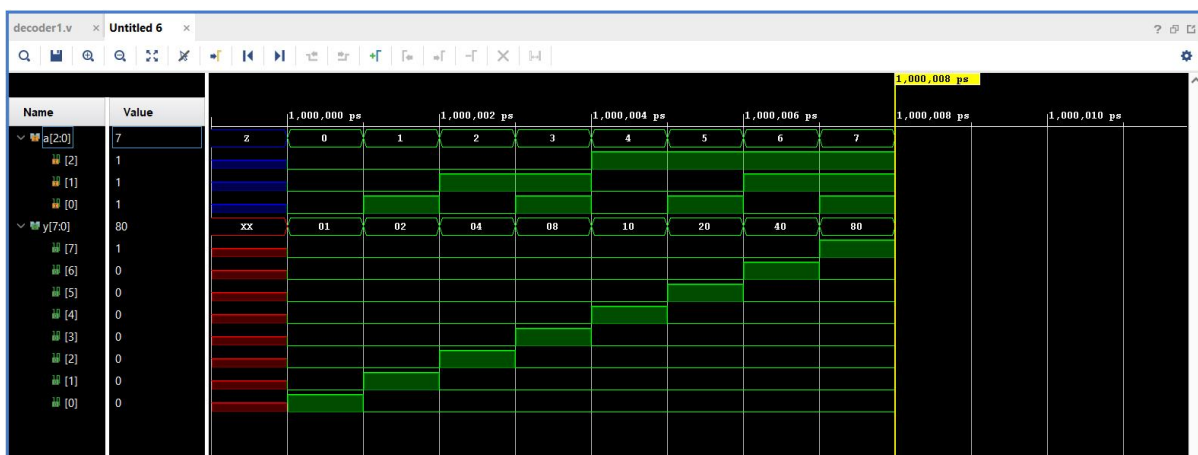

MULTIPLEXER

LOGIC DIAGRAM

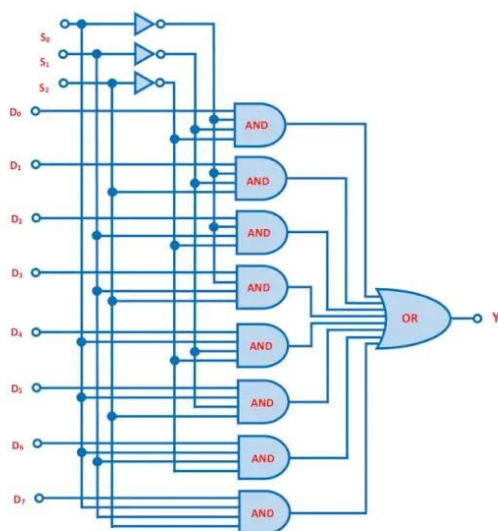

S2	S1	S0	O0	O1	O2	O3	O4	O5	O6	O7
0	0	0	I	0	0	0	0	0	0	0
0	0	1	0	I	0	0	0	0	0	0
0	1	0	0	0	I	0	0	0	0	0
0	1	1	0	0	0	I	0	0	0	0
1	0	0	0	0	0	0	I	0	0	0
1	0	1	0	0	0	0	0	I	0	0
1	1	0	0	0	0	0	0	0	I	0
1	1	1	0	0	0	0	0	0	0	I

VERILOG CODE

```

module mux(s,c,a);
input [2:0]s;
input [7:0]a;
wire [7:0]w;

output c;


and(w[0],a[0],~s[2],~s[1],~s[0]);
and(w[1],a[1],~s[2],~s[1],s[0]);
and(w[2],a[2],~s[2],s[1],~s[0]);
and(w[3],a[3],~s[2],s[1],s[0]);
and(w[4],a[4],s[2],~s[1],~s[0]);
and(w[5],a[5],s[2],~s[1],s[0]);
and(w[6],a[6],s[2],s[1],~s[0]);
and(w[7],a[7],s[2],s[1],s[0]);

or(c,w[0],w[1],w[2],w[3],w[4],w[5],w[6],w[7]);

endmodule


```

OUTPUT WAVEFORM

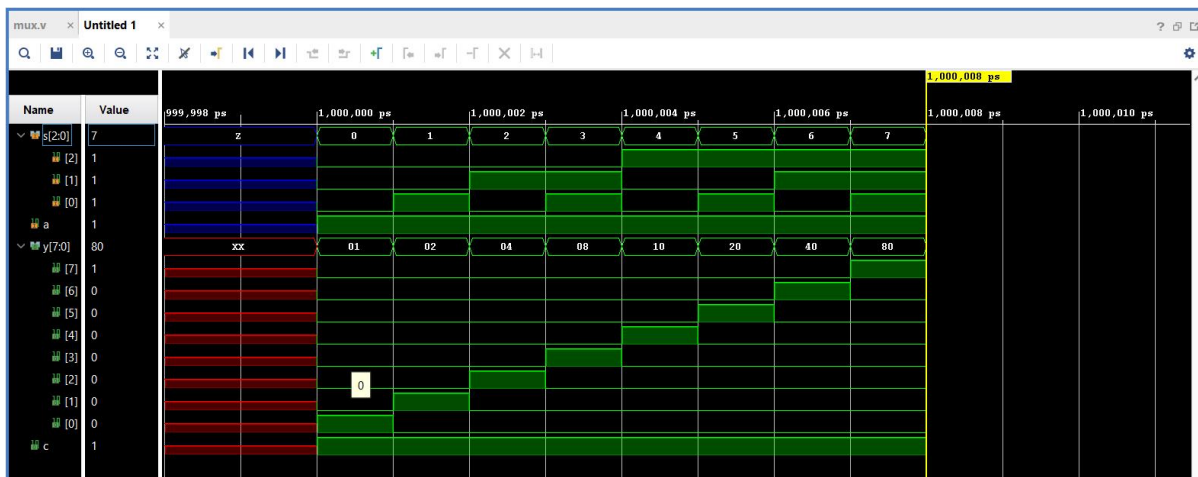

DEMULTIPLEXER

LOGIC DIAGRAM

 

INPUTS			Output							
S ₂	S ₁	S ₀	Y ₇	Y ₆	Y ₅	Y ₄	Y ₃	Y ₂	Y ₁	Y ₀
0	0	0	0	0	0	0	0	0	0	A
0	0	1	0	0	0	0	0	0	A	0
0	1	0	0	0	0	0	0	A	0	0
0	1	1	0	0	0	0	A	0	0	0
1	0	0	0	0	0	A	0	0	0	0
1	0	1	0	0	A	0	0	0	0	0
1	1	0	0	A	0	0	0	0	0	0
1	1	1	A	0	0	0	0	0	0	0

VERILOG CODE

```

module demux_8(s,a,y);
input [2:0]s;
input a;
output [7:0]y;
and(y[0],a,~s[2],~s[1],~s[0]);
and(y[1],a,~s[2],~s[1],s[0]);
and(y[2],a,~s[2],s[1],~s[0]);
and(y[3],a,~s[2],s[1],s[0]);
and(y[4],a,s[2],~s[1],~s[0]);
and(y[5],a,s[2],~s[1],s[0]);
and(y[6],a,s[2],s[1],~s[0]);
and(y[7],a,s[2],s[1],s[0]);
endmodule

```

OUTPUT WAVEFORM



MAGNITUDE COMPARATOR

LOGIC DIAGRAM



Inputs		Outputs		
A	B	A<B	A=B	A>B
00001100	00001100	0	1	0
00001010	00010001	1	0	0
00001111	00000101	0	0	1
00011000	00011000	0	1	0

VERILOG CODE

```
module comparator(a,b,eq,lt,gt);
```

```
input [3:0] a,b;
```

```
output reg eq,lt,gt;
```

always $@(a,b)$

begin

if (a==b)

begin

```
eq = 1'b1;
```

lt = 1'b0;

```
gt = 1'b0;
```

end

```
else if (a>b)
```

begin


```
eq = 1'b0;
```

```

lt = 1'b0;
gt = 1'b1;
end
else
begin
eq = 1'b0;
lt = 1'b1;
gt = 1'b0;
end
end
endmodule

```

OUTPUT WAVEFORM

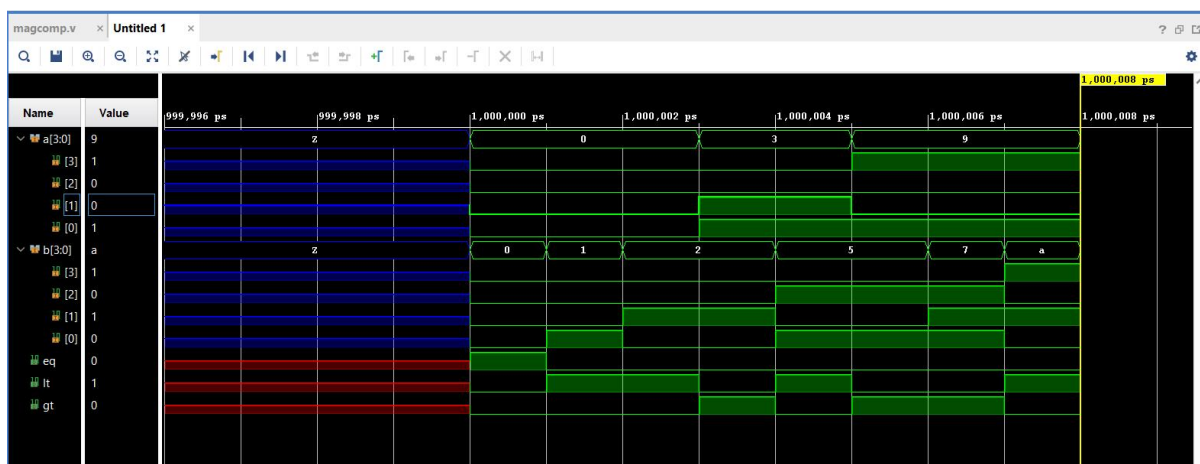

RESULT

Thus the simulation and implementation of combinational logic circuits is done and outputs are verified successfully.